

LAIKIPIA



UNIVERSITY

## UNIVERSITY EXAMINATIONS

SECOND SEMESTER 2023/2024 ACADEMIC YEAR

FOURTH YEAR EXAMINATION FOR THE DEGREE  
BACHELOR OF EDUCATION (SCIENCE) AND  
BACHELOR OF SCIENCE (GENERAL)

PHYS 422: DIGITAL ELECTRONICS

***STREAM: R***

***TIME: 2 HRS***

***DAY: TUESDAY[2.30P.M -4.30P.M]***

***DATE: 16/04/2024***

**THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES**

**PLEASE DO NOT OPEN UNTIL THE INVIGILATOR SAYS SO.**




**INSTRUCTIONS:**

- Read the question paper carefully.
- Answer Question ONE and any other TWO Questions.
- Question **ONE** carries **40 marks** and the other **FOUR** carry **15 marks** each.
- Do not carry mobile phones or any electronic transmission device to the examination room.

**QUESTION ONE (40 MARKS)**

 - (a) Define the following terms as used in Digital Electronics:
- Code
  - Bit
  - Digitization **(3 Marks)**
- (b) (i) Verify that a two level AND – OR topology is equivalent to a NAND – NAND system **(4 Marks)**
- (ii) Convert the decimal number 274.1875 to their binary equivalent. **(4 Marks)**
- (iii) Convert the hexadecimal number  $7C9_{16}$  to their decimal equivalents: **(2 Marks)**
- (c) Give two advantages of digital signals **(2 Marks)**
- (d) Solve the following in Hexadecimal
- $0300 - 005A$
  - $91B + 6F2$  **(4 Marks)**
- (e) Adopt a 6 bit notation to perform arithmetic operations of the following decimal numbers in Binary, and confirm the answer
- (i)  $24 + 26$  (ii)  $+9 - 13$  (iii)  $-5 - 13$  **(6 Marks)**
- (f). Use J-K flip flops and other relevant logic gates to design an asynchronous decade counter. How would the circuit of the asynchronous decade counter be modified into a synchronous decade counter? **(6 Marks)**
- (g). What are the advantages of digital signals over analog signals? **(3 Marks)**
- (h). (i) Simplify the logic circuit shown below. **(4 Marks)**





(ii) Draw the logic diagram of the simplified circuit in (i) above using NAND gates only. (2 Marks)

**QUESTION TWO (15 MARKS)**

(a) Convert the binary number 11111001100 to its equivalent decimal number (3 Marks)

(b) A person claims to be born in 7C8<sub>hex</sub> year. What is his actual age in binary and decimal systems? (4 Marks)

(c) Convert the following Boolean expression into standard POS form:


$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D) \quad (5 \text{ Marks})$$

(d) Use the Karnaugh map to minimize the following standard SOP expression:

$$A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} \quad (3 \text{ Marks})$$

**QUESTION THREE (15 MARKS)**

 (a) Consider the logic gate circuit diagram below.



- (i) Write the Boolean expression for the logic circuit (2 Marks)
- (ii) Obtain the truth table in binary numbers for the logic circuit (3 Marks)
- (b) Determine the binary values of the variables for which the following standard SOP expression is equal to zero  $(A + B + C + D)(A + \bar{B} + \bar{C} + D)(\bar{A} + B + \bar{C} + \bar{D})$  (4 Marks)
- (c) Show how a computer would multiply the binary numbers 1001 and 1011 which are in 2's compliment. Assume MSB is a sign bit. (3 Marks)
- (d) (i) Differentiate between an Excess-3 code and a Gray- code. (1 Mark)
- (ii) Convert the following binary numbers to Gray- code (a). 110100 (b). 101101 (2 Marks)

**QUESTION FOUR (15 MARKS)**


- (a) Draw the logic circuit represented by the expression  $Y = A\bar{B}C + AB\bar{C}$  (2 Marks)
- (b) Given the expression:  $Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C} + ABC$ . Obtain a minimized expression using K-map (3 Marks)
- (c) (i). Differentiate between SRAM and DRAM (2 Marks)
- (ii). What is the advantage of a computer with many registers over the one with few (1 Mark)
- (iii). Define an analogue signal (1 Mark)

(d). Draw a labelled block diagram of a complete 4-bit parallel adder with registers capable of ADD and SUBTRACT operations. **(6 Marks)**


**QUESTION FIVE (15 MARKS)**

(a) Using NAND gates draw a logic symbol of a clocked SR flip-flop. Briefly explain the operation of the clocked SR flip-flop. **(6 Marks)**

 5. (b). (i). The waveforms in Fig. 1 are applied to the J, K, in Fig. 2 and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET. **(5 Marks)**



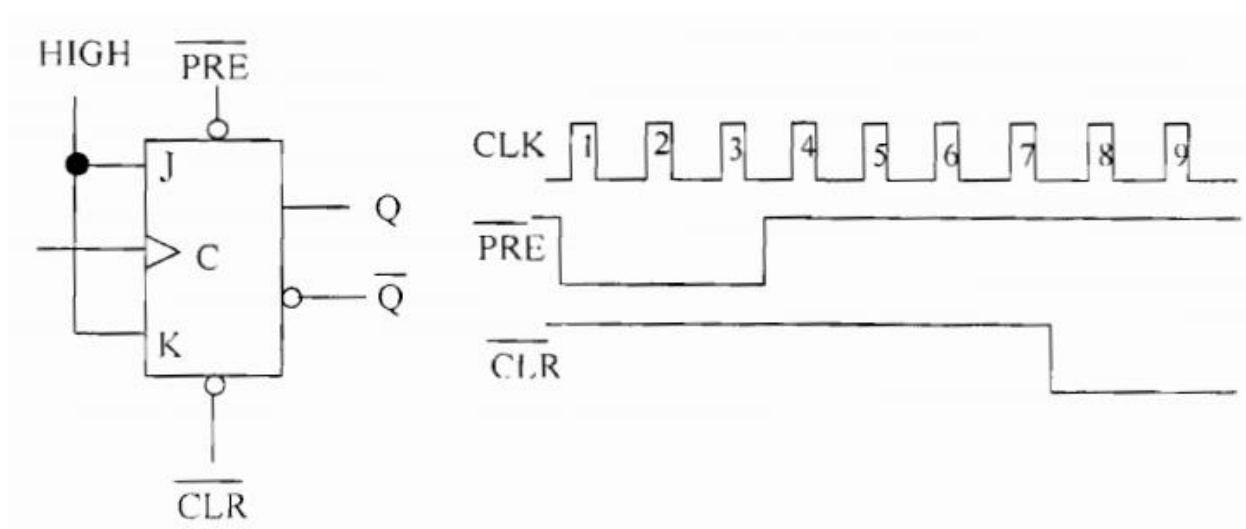5. (b). (ii). For the positive edge triggered J-K flip flop with preset and clear inputs in the Figure below, determine the Q output for the inputs shown in the timing diagram if Q is initially LOW.



**(4 Marks)**